

9 Month Program

Digital IC Design Track


Project (2)

“Flip-Flop Design and Characterization”

Instructor: Dr Hesham Omran


Part One: Flip-Flop Component Schematics:

Inverter Schematic:

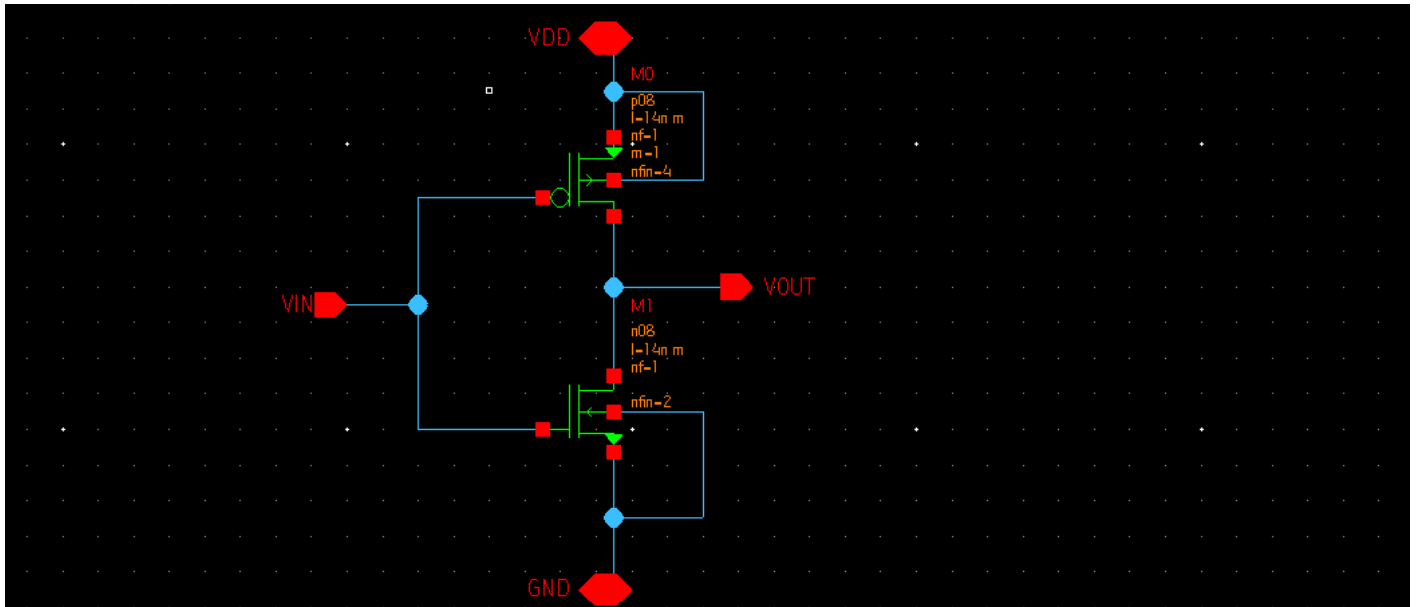


By cpressing Q: we set nfin of pfet to 4 & nfet to 2.


Inverter Symbol:

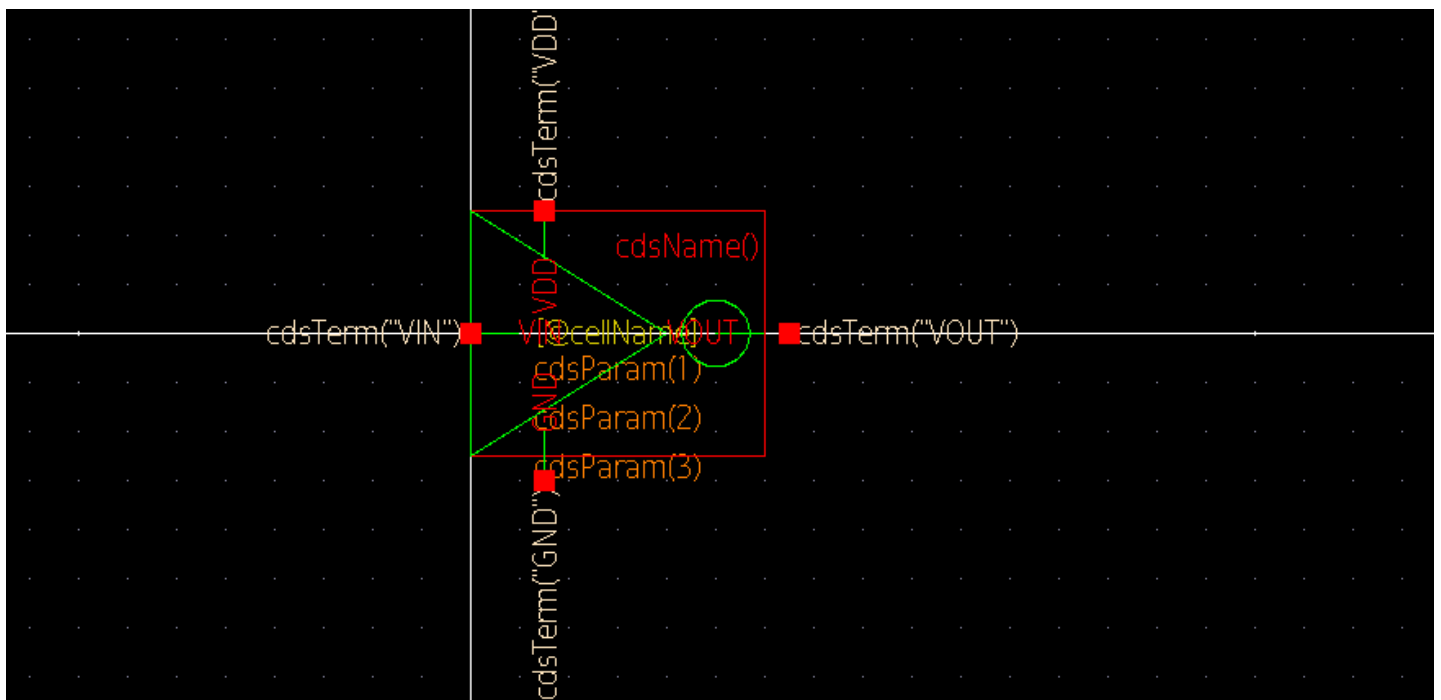


Transmission Gate Schematic:

 


Transmission Gate Symbol:

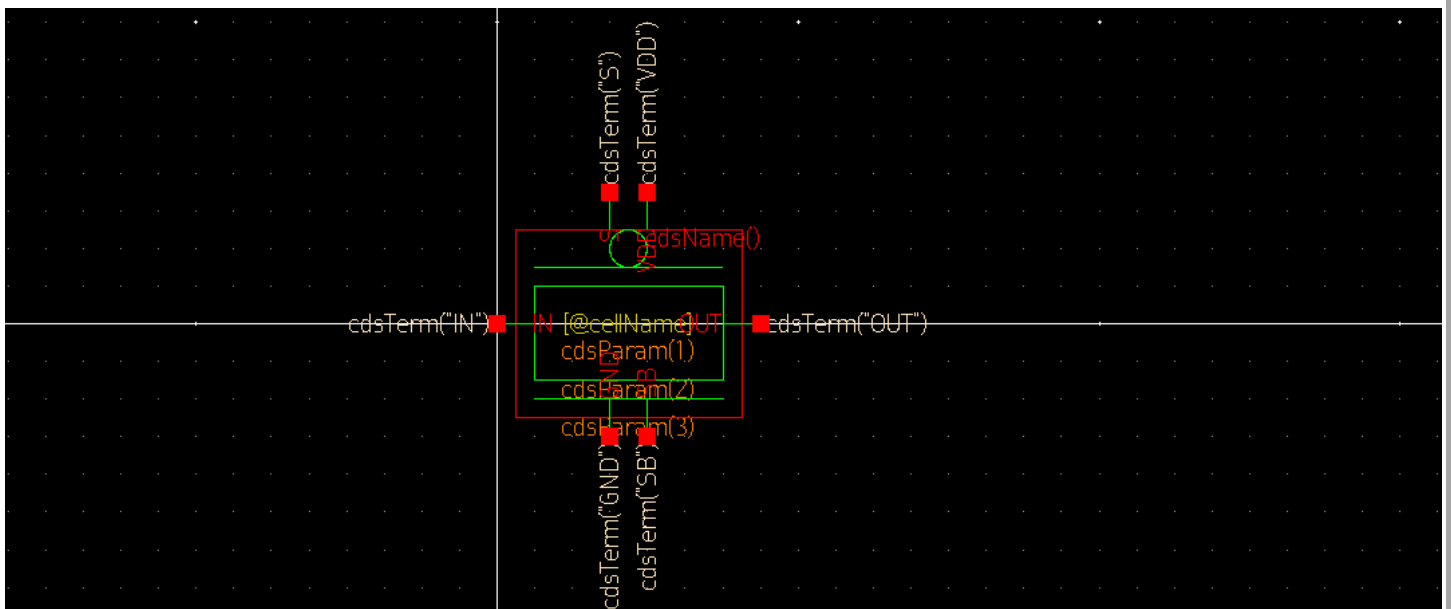




Tri-State Buffer Schematic:

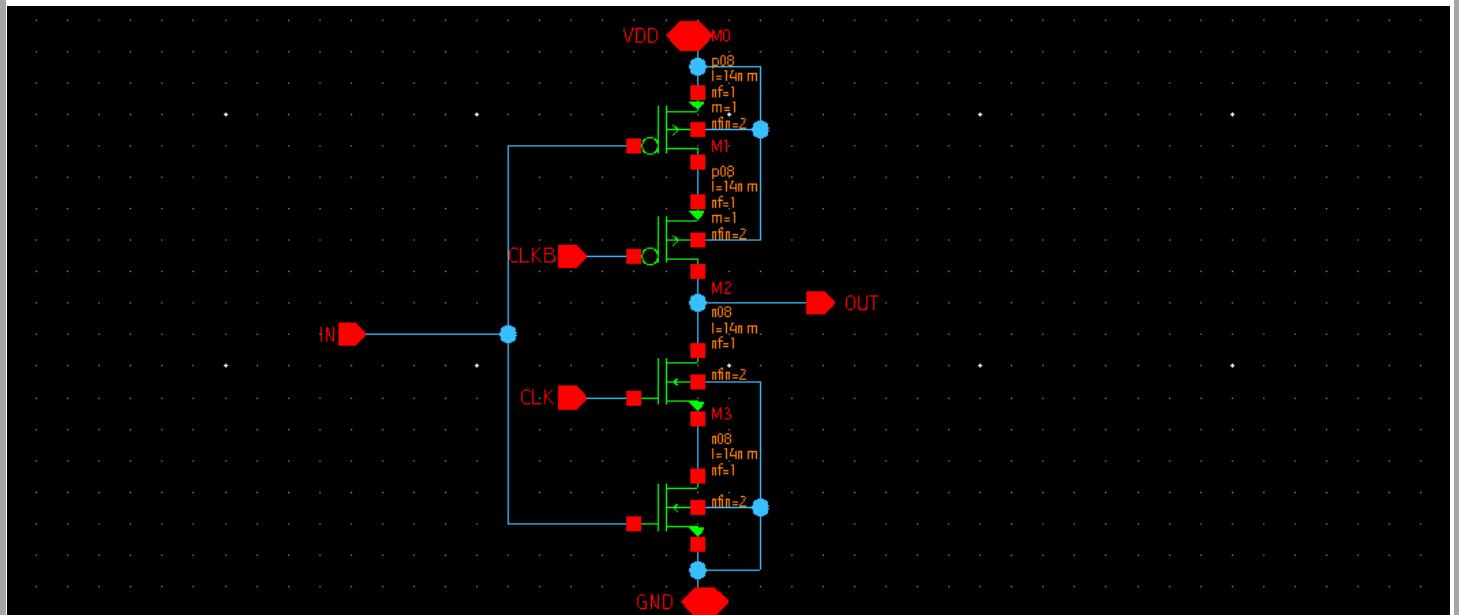


Tri-State Buffer Symbol:

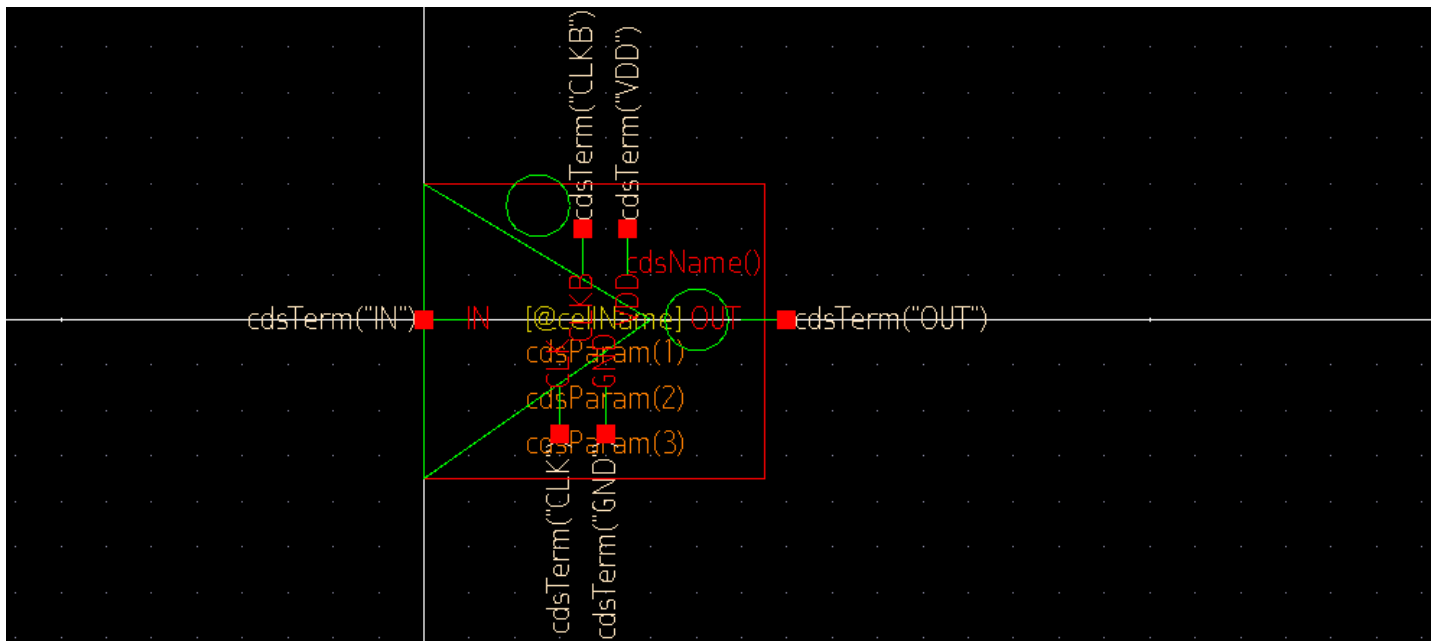


Flip-Flop Schematic:

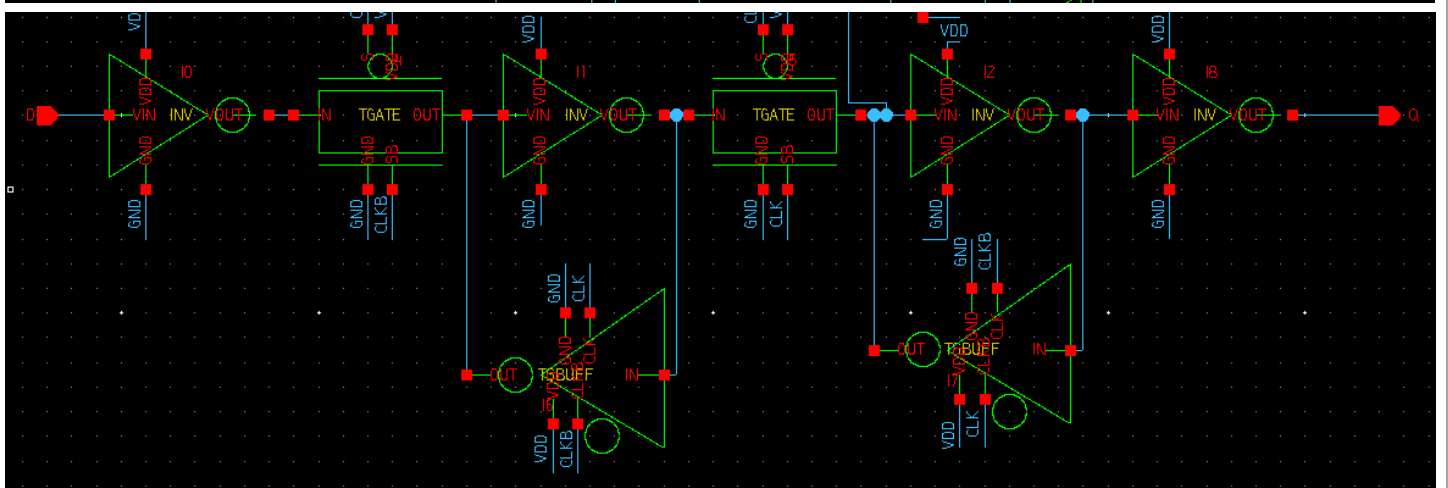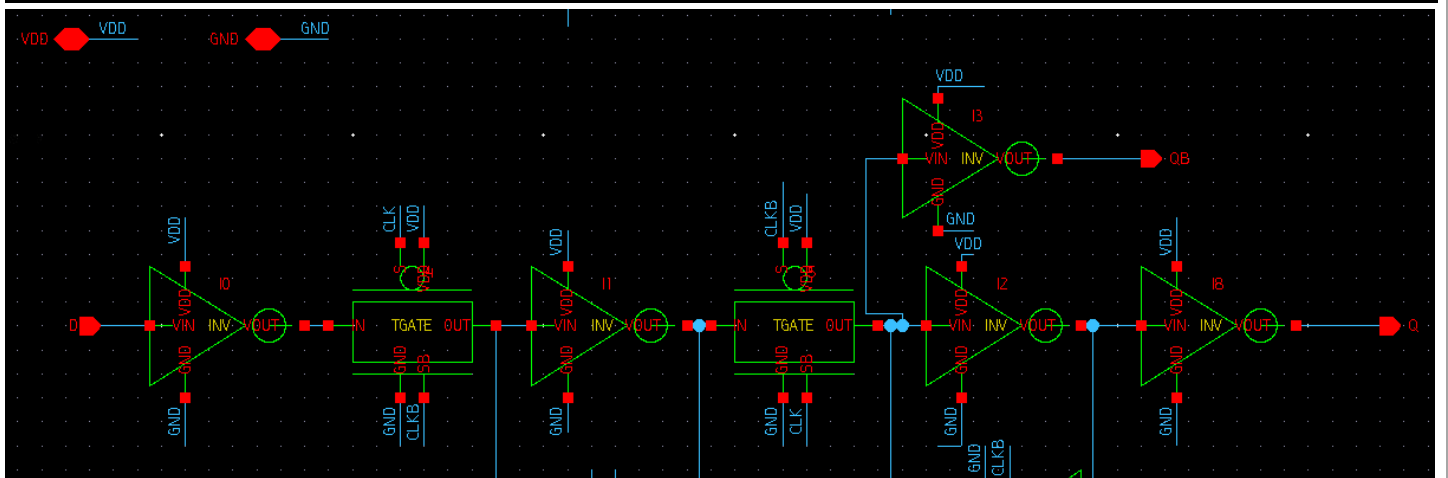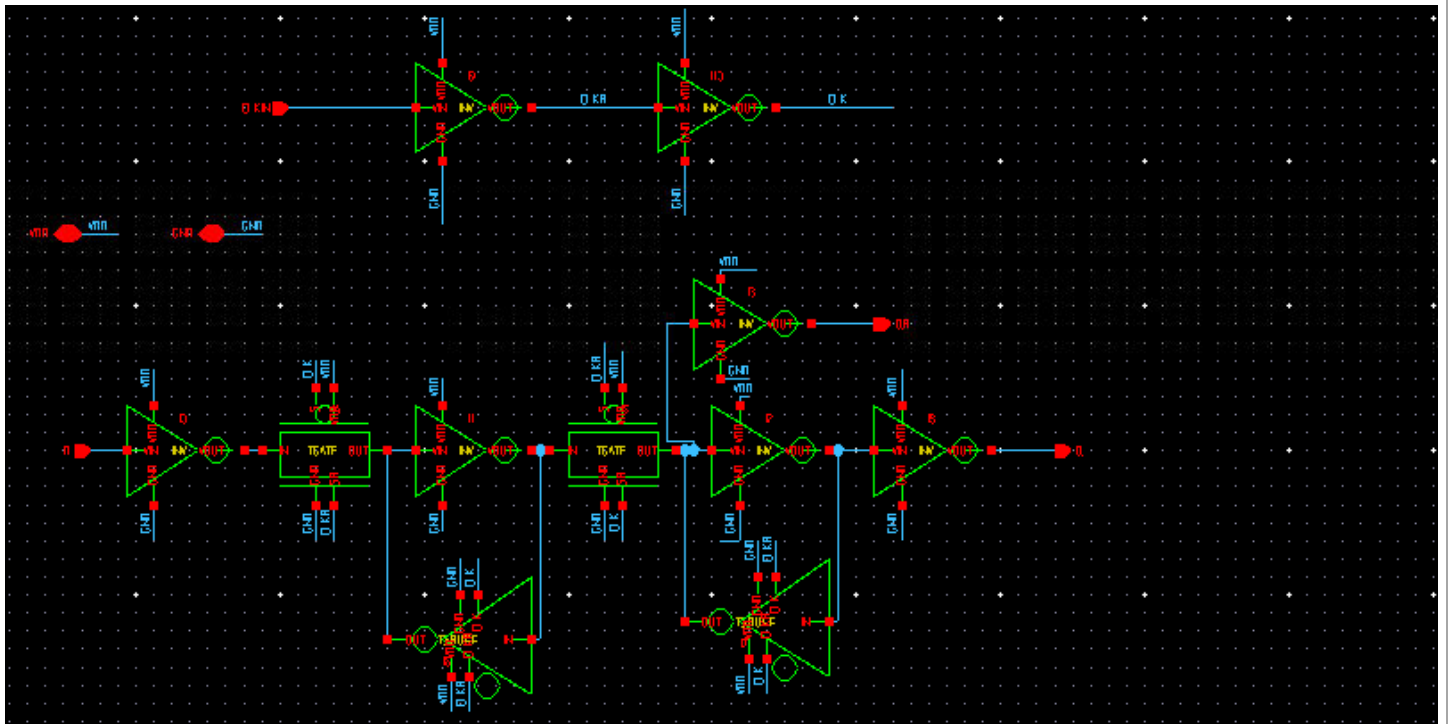

Flip-Flop Symbol:

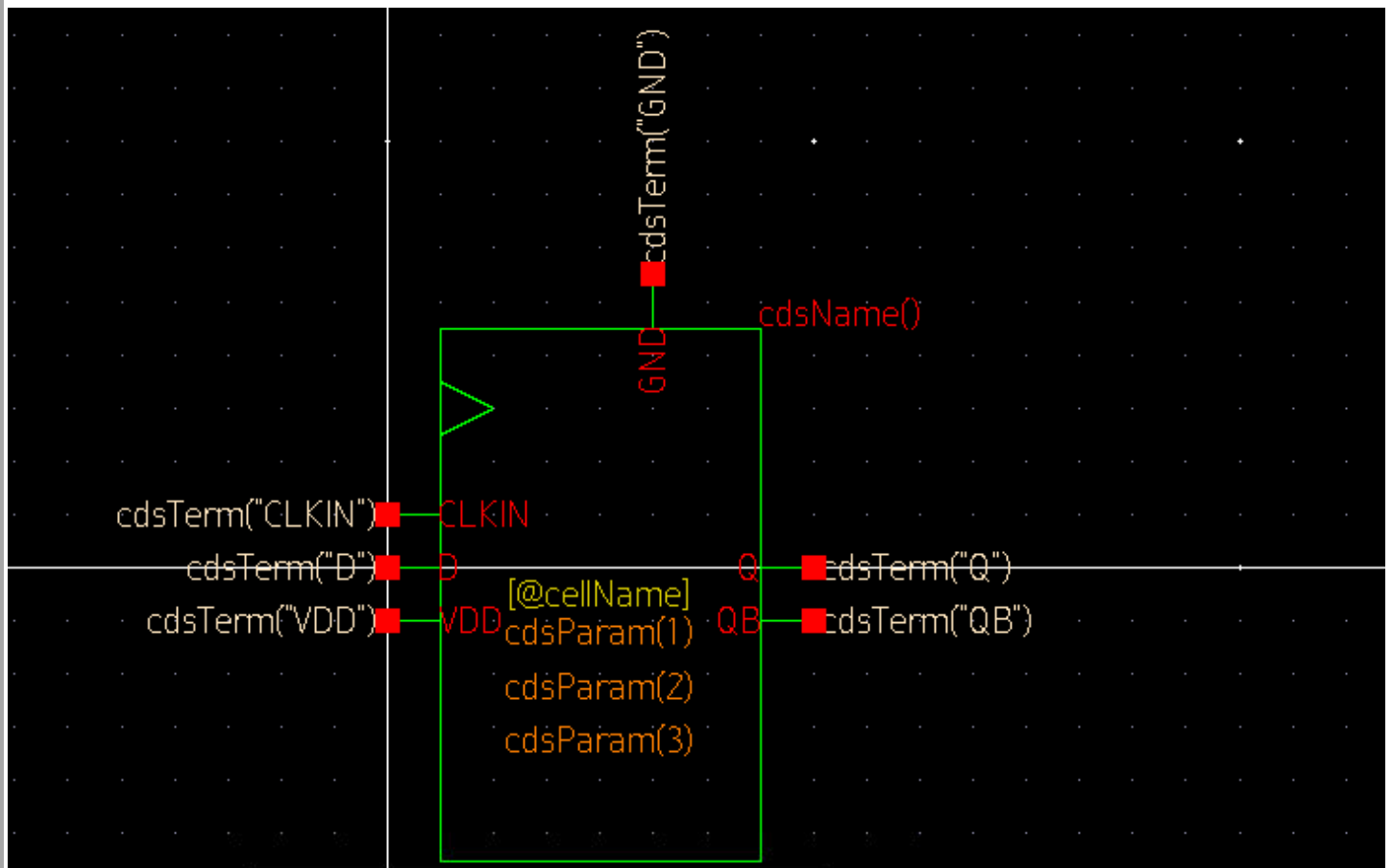

Part Two: Flip-Flop Testbench:

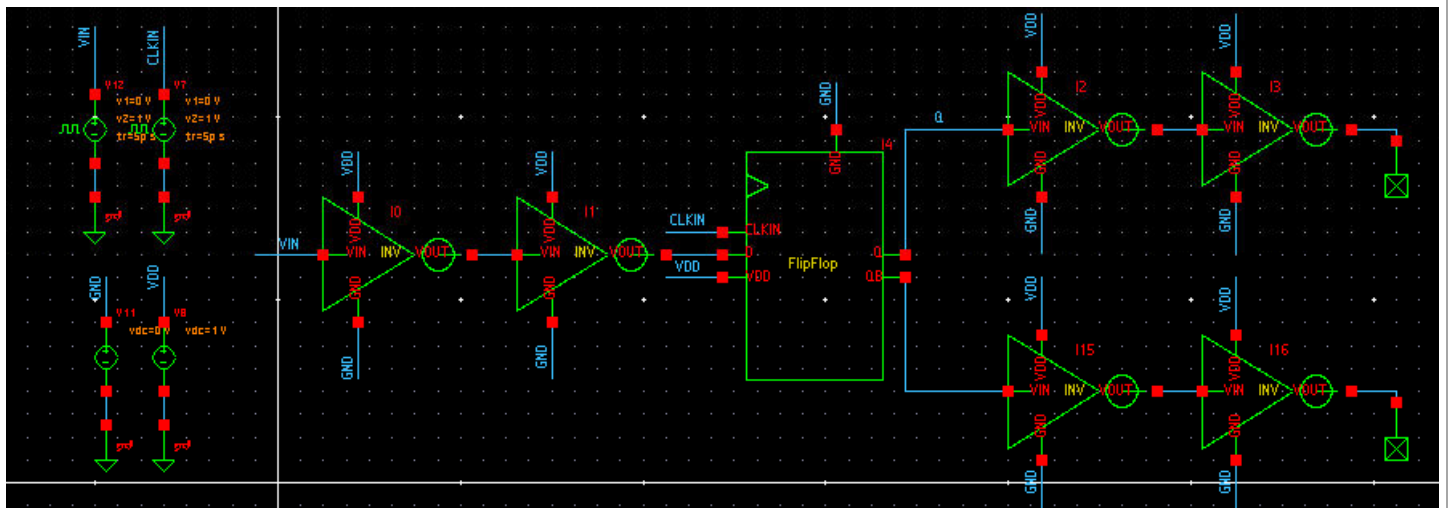

Here we were asked to shape the input & the output, thus two inverters were used for every input & output.

Now for setting the vpulse sources for the input & clock:

Clock Pulse: The period was set to 70p s because we were asked to set the clock pulse to $10 \cdot FO4$ & $FO4$ is $= L_{min}/2$. Since we're working on 14nm tech so $FO4 = 7$. The pulse width = Period/2.

Trise & Tfall were set to 5p s as a reasonable value that we usually use.


The Input signal pulse was set according to the lab requirements in the sheet.

Transient Analysis:

▶ tran tran ☒ Start Time: 0 Time Step: 1p Stop Time: 140p

Note: Stop time in the results is set to 1200p s to see 4 input pulses in the plot.


The Resulting Waveform:

 

Note: Net3 Represents Q & Net4 Represents Q_Bar. Notice that in every positive clock edge after the input rises to 1, the output Q rises to 1 & Q_Bar falls to 0.

Part Three: Delay

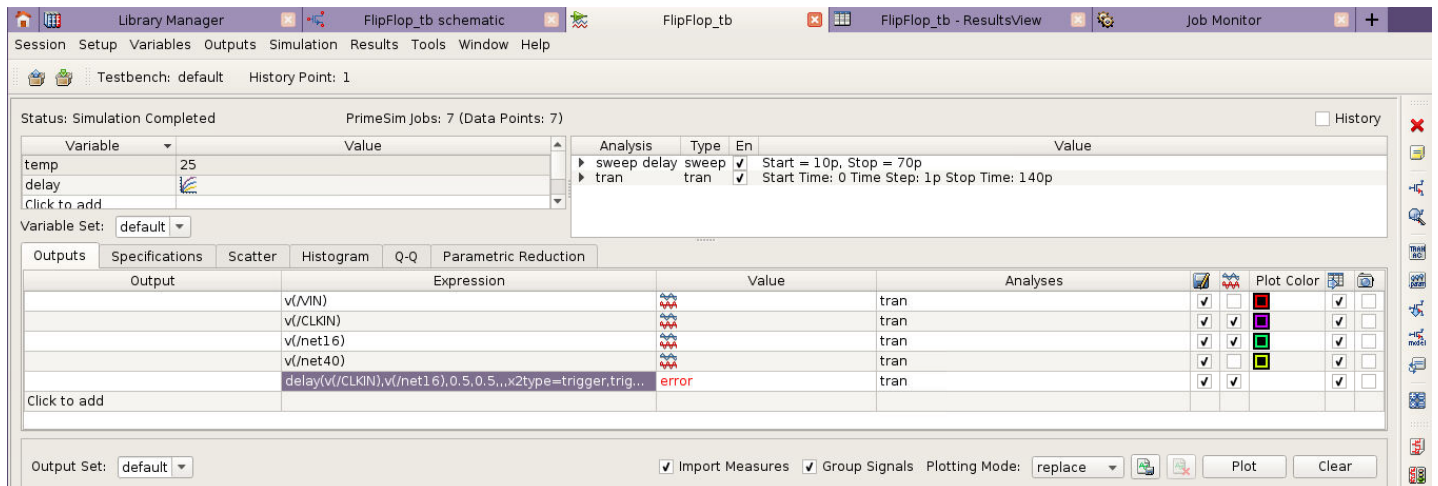First Trial: Setting the delay equation in the “Expression” part & running a parametric sweep on a delay parameter set to the input pulse: 10p:10p:70p.




The resulting delay values were as follows:

Violations	Min	Max	delay 10p	delay 20p	delay 30p	delay 40p	delay 50p	delay 60p
< Filter	< Filter	< Filter	< Filter	< Filter	< Filter	< Filter	< Filter	< Filter
1	12.2185p	12.2599p	12.2538p	12.2541p	12.2599p	12.2315p	12.2495p	12.2185p

But it was more reasonable to set the delay variable for the clock, so next I set a delay variable called tdc to the clock & set that of the input to 0. The tdc variable was swept to 10p:10p:70p as well.

Next I added the tdc expression to primewave.

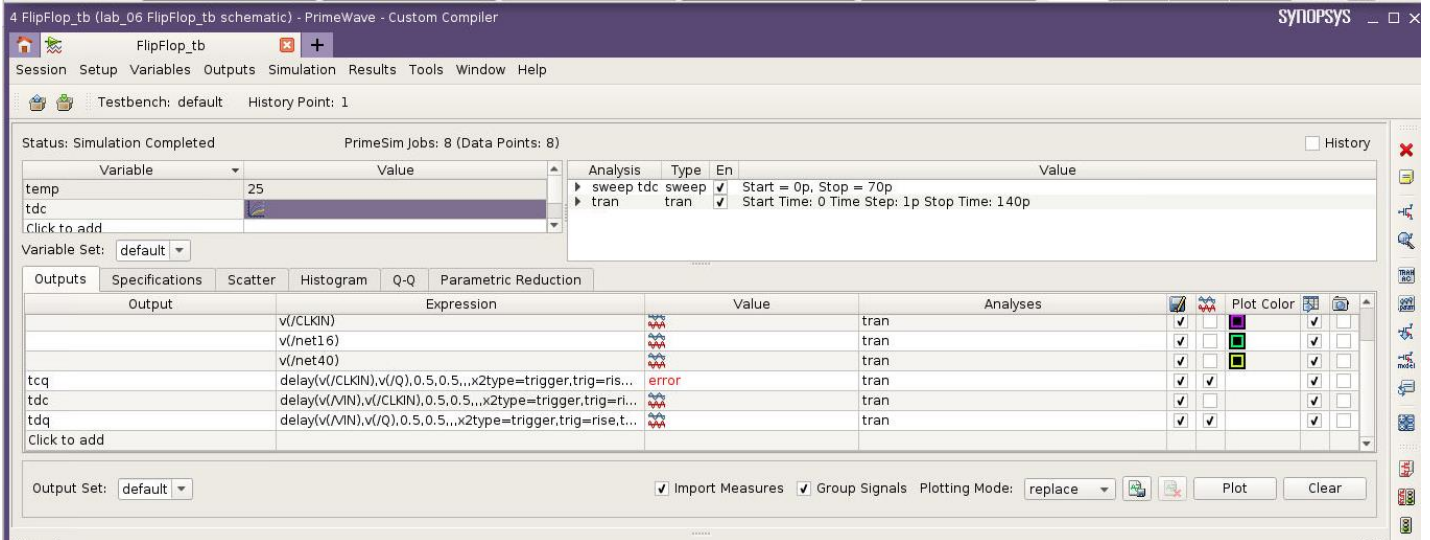Moreover, I added two variables to the output & set their expressions as well (The same expression but with changing the evaluated terms). As shown below:



The expressions are shown here:

tcq:


delay(v(/CLKIN),v(/Q),0.5,0.5,,,x2type=trigger,trig=rise,target=either,occu=multiple)

tdc:


delay(v(/VIN),v(/CLKIN),0.5,0.5,,,x2type=trigger,trig=rise,target=either,occu=multiple)

tdq:

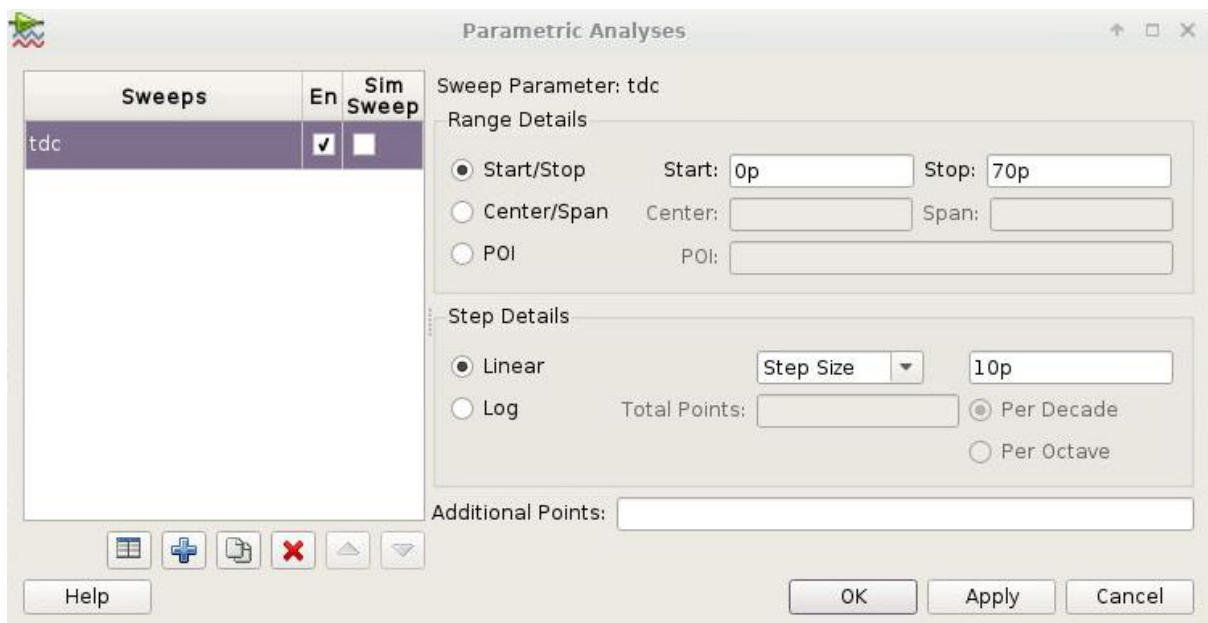delay(v(/VIN),v(/Q),0.5,0.5,,,x2type=trigger,trig=rise,target=either,occu=multiple)



 This was the resulting plot: It seems reasonable and close to what we've happened to study in the lecture.



Now using the measurement tool & Data(x,y) to get the delay values which happened to be:

$T_{ccq} = 10.8 \text{ p s}$ & to get it in terms of FO4 we divide this value by 7.

$T_{pcq} = 10.9 \text{ ps}$

T_{setup} (The point on x at which the slope = -1) = 9.98 p s .

If it's needed, here are the delay values for different points in the plot:

Consolidated Pass/Fail													
Testbench	Equations	Specification	Violations	Min	Max	tdc 0	tdc 10p	tdc 20p					
Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter	Filter
default	tcq:tran		0	10.7453p	80.7861p	80.7861p	10.7453p	10.7905p					
	tdc:tran		0	0	70p	0	10p	20p					
	tdq:tran		0	20.7453p	80.7872p	80.7861p	20.7453p	30.7905p					

	tdc 30p	tdc 40p	tdc 50p	tdc 60p	tdc 70p
Filter	Filter	Filter	Filter	Filter	Filter
	10.7651p	10.7969p	10.7845p	10.7933p	10.7872p
	30p	40p	50p	60p	70p
	40.7651p	50.7969p	60.7845p	70.7933p	80.7872p